


∴ Current Electricity :-

∴ (Rate of flow of electric charge across a cross-section of conductor)

∴ $i = \frac{\Delta q}{\Delta t}$ $\begin{cases} \rightarrow \text{Scalar Quantity} \\ \rightarrow \text{Ampere (CA)} \end{cases}$

direction of current

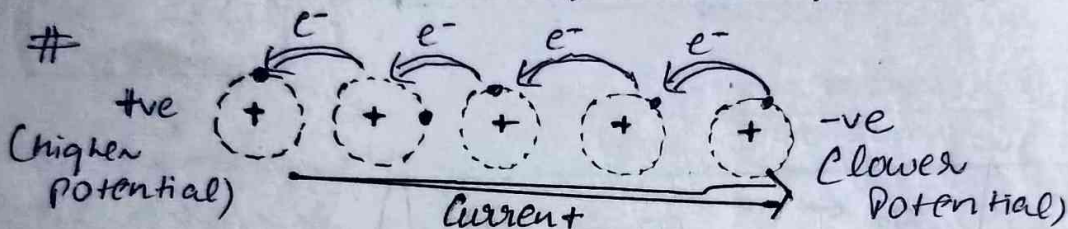
> direction of current is opposite to motion of e^- and moves in the direction of motion of positive charge



> Current density :- (\vec{J})
(Current per unit area)

∴ $J = \frac{di}{dA}$

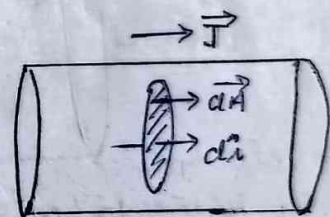∴ Its direction is along the current which passes through that point!




Current density is equal to current / area taken \perp to direction of current!

$J = \frac{di}{(dA \cos \theta)}$

$di = J dA \cos \theta$

$di = \vec{J} \cdot d\vec{A}$



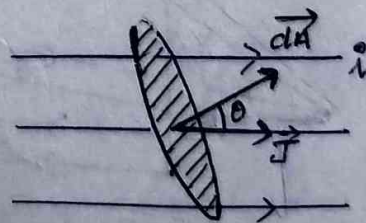


∴ θ angle b/w \vec{J} and $d\vec{A}$

∴ $i = \int \vec{J} \cdot d\vec{A}$

> Drift Speed:-

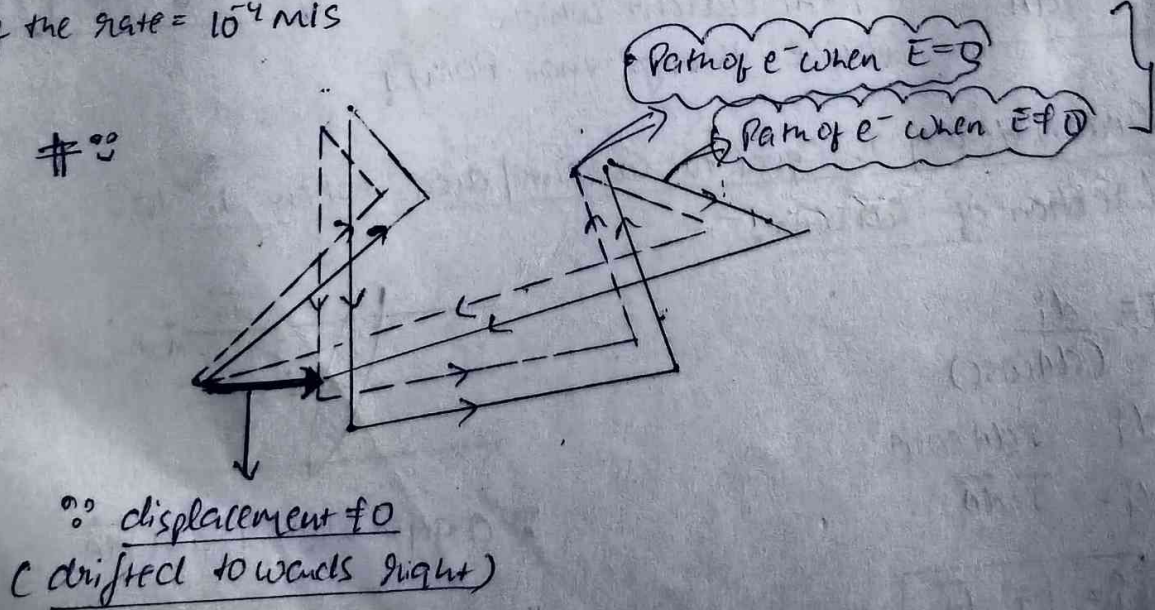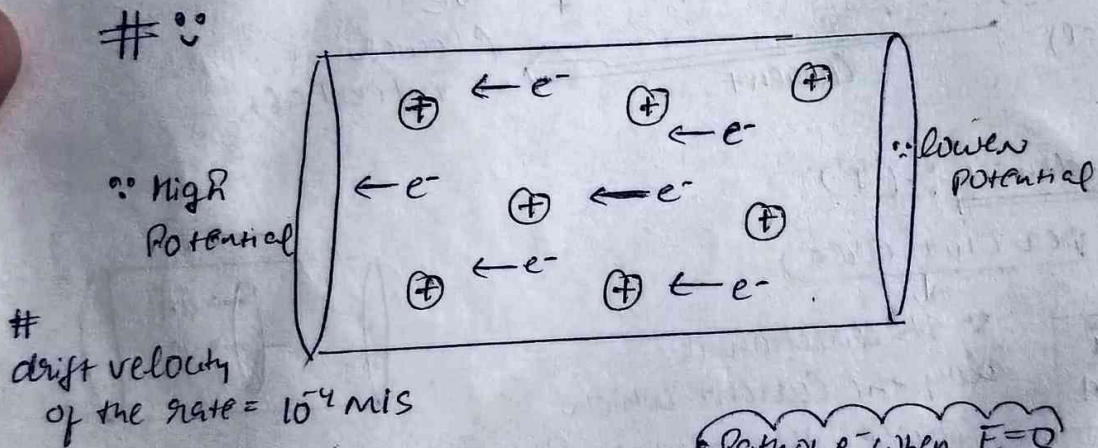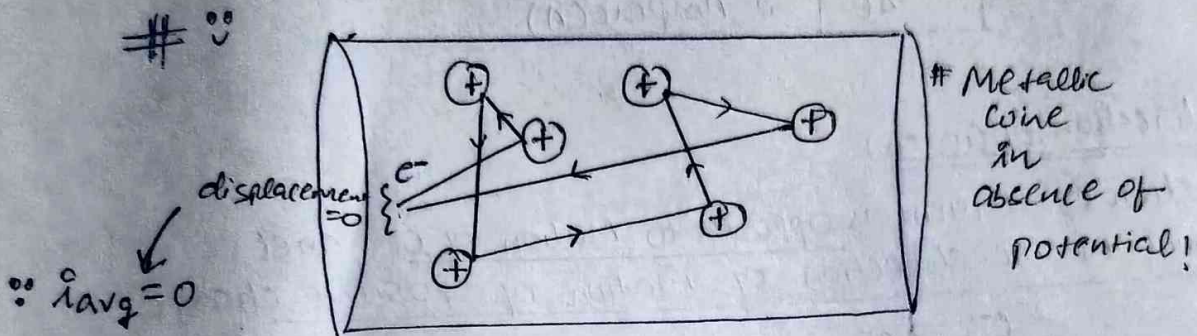∴ The free e^- collide with fixed +ve ion and follow zigzag path so no net flow charge in any direction!



$$F = qE$$

$$F = eE \quad \text{--- (1)}$$

And

$$ma = eE$$

$$a = \frac{eE}{m} \quad \text{--- (2)}$$

$$\vec{a} = \frac{(-e)E}{m}$$

and

$$v = u + at$$

$$v_d = (0) + at$$

$$\therefore \boxed{v_d = \frac{eE(t)}{m}}$$

"Material Specific"

If $d \downarrow \downarrow$ then $\tau \downarrow \downarrow$

And v_d decrease!

> Reltn Btw τ and v_d :-

$$\text{length of Conductor} = l$$

$$\text{free } e^- / \text{unit volume} = n$$

$$\text{Volume of Conductor} = Al$$

Now,

$$n = \frac{N}{Al} \quad (N = \text{total free } e^-)$$

$$N = nAl$$

$$\Delta q = N(e) = nAle$$


$$\Delta q = nAe(elt) \quad \text{--- (1)}$$

$$\text{and } v_d = \frac{l}{\Delta t} \quad \text{--- (2)}$$

from eq 1 and 2,

$$\Delta q = nAe(v_d \Delta t)$$
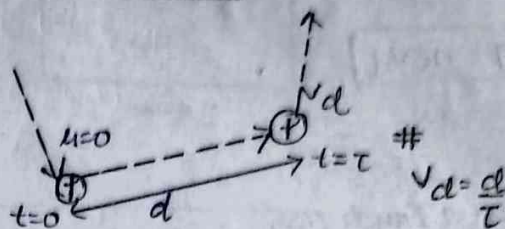
$$\therefore i_{avg} = \frac{\Delta q}{\Delta t} = nAe v_d$$



∴ τ = relaxation time

(Time take b/w two successive collision)

∴ d = Avg distance b/w two successive collision

And

$$J = \frac{i}{A} = \frac{n e A v_d}{A} = n e v_d$$


$$J = n e v_d$$

$$\therefore \boxed{J = n e v_d}$$

for a Conductor;

Current does not change with change in cross-section Area!

$$\therefore \boxed{i_{in} = i_{out}}$$

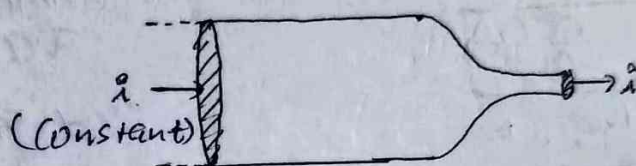

While, \vec{E} , J , V_d do not remain constant

> Ohm's LAW:-

Mobility:- drift speed per unit \vec{E} ; $\boxed{\mu = \frac{v_d}{E}}$

> Deriving Ohm's LAW:-

$$J = n e v_d \text{ and } v_d = \frac{e E \tau}{m}$$

$$J = n e \left(\frac{e E \tau}{m} \right) = \left(\frac{n e^2 \tau}{m} \right) E$$

$$J = \left(\frac{n e^2 \tau}{m} \right) E$$

$$\therefore \boxed{J = \sigma E} ; \sigma = \text{Conductivity} \\ (\text{depends on Material})$$

#

$$\therefore \sigma = \frac{1}{\rho} = \frac{n e^2 \tau}{m} ; \begin{array}{l} \sigma :- \text{Conductivity} \\ \rho :- \text{Resistivity} \end{array}$$

?? $J = \sigma E \rightarrow V = iR$


$$J = \frac{i}{A} = \sigma E$$

$$\Rightarrow \frac{i}{A} = \sigma \left(\frac{V}{l} \right)$$

$$V = i \left(\frac{l}{\sigma A} \right)$$

$$V = i \left(\frac{\rho l}{A} \right) \because \rho = \frac{1}{\sigma}$$

∴ $V = iR$ where $R = \frac{\rho l}{A}$

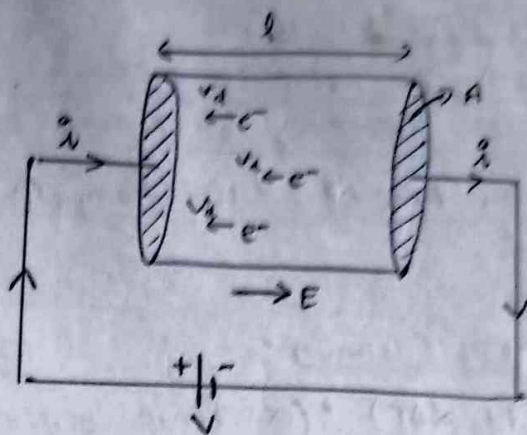


> Conductance :- (G)

(Reciprocal of resistance)


$$G = \frac{1}{R} = \frac{A}{\rho l}$$

∴ $G = \frac{A}{\rho l}$

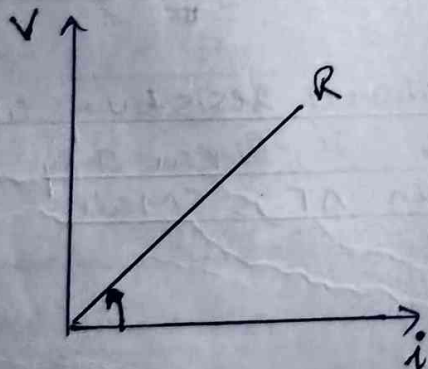

∴ Ohmic Conductor

∴ $R = \frac{V}{I}$

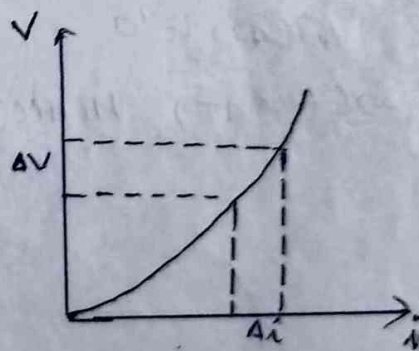

∴ Non-ohmic Conductor

∴ $R = \frac{\Delta V}{\Delta i}$

> Effect of Temperature:-

(As Temp \uparrow , it increase thermal agitation due to which rate of collision increase, the relaxation time \downarrow ; resistivity \uparrow & resistance \uparrow also)

> Variation of S with T :-

$$S = S_0(1 + \alpha \Delta T) \quad ; \quad (\alpha = \text{Temp. Coefficient of resistivity})$$

> Variation of R with T :-

•• Considering dimension to be invariant
($\Delta T \rightarrow$ small)

$$R = R_0(1 + \alpha \Delta T) \quad ; \quad (R = \text{resistance of conductor})$$



$$\# \left[S = S_0(1 + \alpha \Delta T + \beta (\Delta T)^2) \right]$$

$$\Rightarrow \text{for } (\Delta T)^2 \ll \Delta T$$

$$\Rightarrow \text{so, } \beta (\Delta T)^2 \ll \alpha \Delta T$$

$$\Rightarrow \beta (\Delta T)^2 \approx 0$$
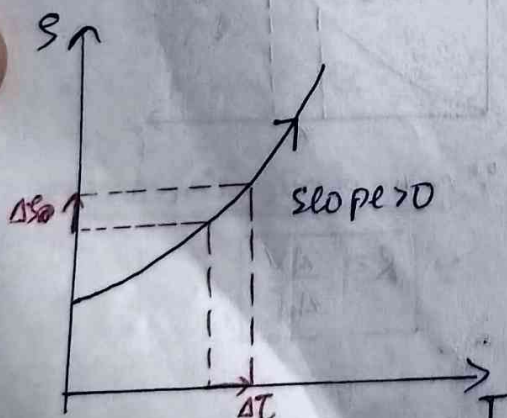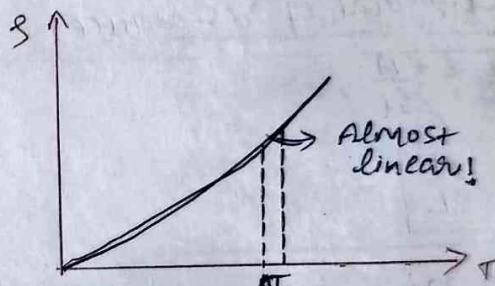
$$\Rightarrow S = S_0(1 + \alpha \Delta T) \quad \text{Hence; Variation of resistivity with Temp is linear only. When } \Delta T \text{ is small}$$




Metals

$$S = S_0(1 + \alpha \Delta T)$$

$$\alpha = \frac{S - S_0}{S_0 \Delta T} = \frac{1}{S_0} \left(\frac{\Delta S}{\Delta T} \right)$$
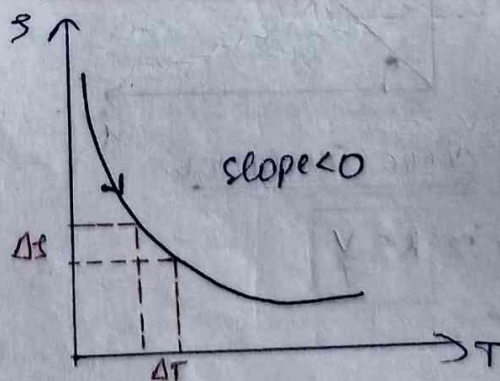
$$\alpha = \frac{1}{S_0} (\tan \theta) \Rightarrow \boxed{\alpha > 0}$$



N-Metals

$$\alpha = \frac{1}{S_0} (\tan \theta)$$

$$\boxed{\alpha < 0}$$

for semi conductors;


Conductivity decreases with decrease in Temp
or Resistivity decrease with Temp. (↑)

∴ Temp. (↑) → holes (↑) → σ (↑) → S (↓)

for Alloys, ρ always remains constant with Temperature
(V-v-low Temp. coefficient)

> Series Combination :-

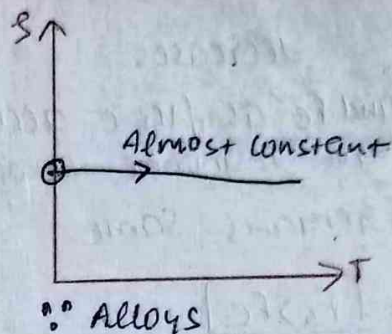
$$\boxed{R_{eq} = R_1 + R_2 + R_3 \dots}$$



Superconductor offer zero resistance at critical temperature.

> Parallel Combination :-
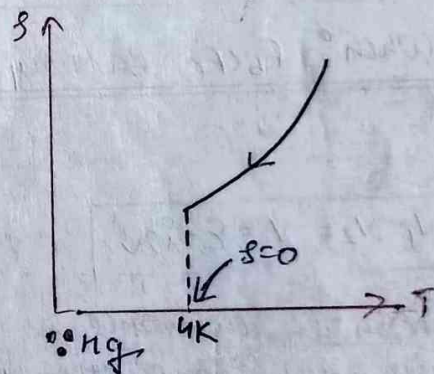
$$\boxed{\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



> Concept of Battery :-

C Internal force due to Battery
mechanism makes charge inside the Battery move


∴ in steady state;

$$F_b = F_E = qE$$

(e is in equilibrium)

$$W_{Battery} \Rightarrow F_b \times d \Rightarrow (qE)d \Rightarrow q(\mathcal{E}d)$$

$$\boxed{\therefore W_{Battery} = qV}$$

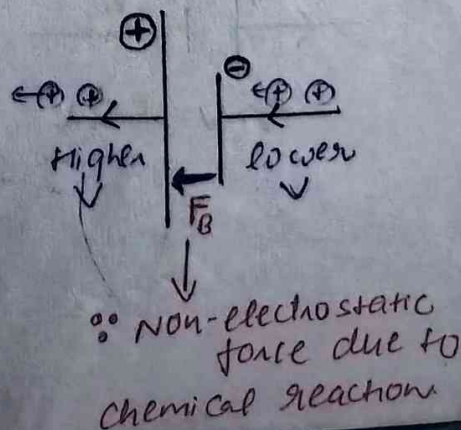

EMF: (\mathcal{E}) Potential diff b/w its terminal when not connected externally.

Work done by the Battery per unit charge

$$\mathcal{E} = \frac{W_{\text{Battery}}}{q} = \frac{qV}{q} = V$$

$$\boxed{\mathcal{E} = V}$$

decreases


\mathcal{E} and f_e as free e^- accumulate on the terminal however,

F_b remains same.

So:

$$\boxed{F_b > f_e}$$

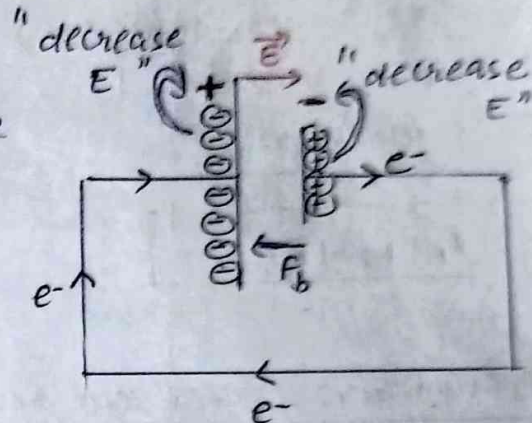
Battery drives $-ve$ charge from $+$ ve to $-ve$ terminal.



When F_b < f_e Battery stops working

$$\boxed{V_1 - V_2 = V = \mathcal{E} - i r}$$

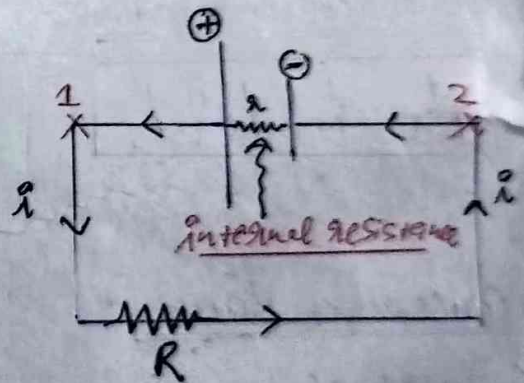Internal resistance is resistance offered by conductor inside Battery!



(I)

$$V = \mathcal{E} - i r$$

(II)

$$V = \mathcal{E} + i r$$


> Cells in series :-

$$V_1 = \mathcal{E}_1 - i r_1 \quad \text{--- (1)}$$

$$V_2 = \mathcal{E}_2 - i r_2 \quad \text{--- (2)}$$

$$V_3 = \mathcal{E}_3 - i r_3 \quad \text{--- (3)}$$
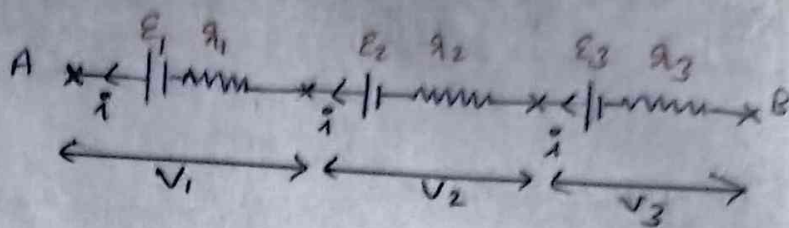
$$V_{AB} = \mathcal{E}_{eq} - i r_{eq} \quad \text{--- (4)}$$



In series,

$$V_{AB} = V_1 + V_2 + V_3$$

$$\mathcal{E}_{eq} - i r_{eq} = (\mathcal{E}_1 - i r_1) + (\mathcal{E}_2 - i r_2) + (\mathcal{E}_3 - i r_3)$$


$$\mathcal{E}_{eq} - i r_{eq} = (\mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3) - i(r_1 + r_2 + r_3)$$

By comparing,

$$\boxed{\mathcal{E}_{eq} = \mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3}$$


$$\boxed{r_{eq} = r_1 + r_2 + r_3}$$

#

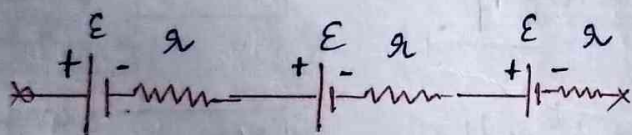

$$> \mathcal{E}_{eq} = (\mathcal{E} + \mathcal{E} + \mathcal{E}) = 3\mathcal{E}$$

$$> r_{eq} = (r + r + r) = 3r$$

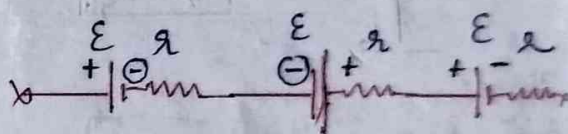

$$> \mathcal{E}_{eq} = (\mathcal{E} - \mathcal{E} + \mathcal{E}) = \mathcal{E}$$

$$> r_{eq} = (r + r + r) = 3r$$

> Cells in Parallel :-

$$V = \mathcal{E}_1 - i_1 r_1 \Rightarrow i_1 = \left(\frac{\mathcal{E}_1}{r_1} - \frac{V}{r_1} \right) \quad \text{--- (1)}$$

$$V = \mathcal{E}_2 - i_2 r_2 \Rightarrow i_2 = \left(\frac{\mathcal{E}_2}{r_2} - \frac{V}{r_2} \right) \quad \text{--- (2)}$$

$$V = \mathcal{E}_3 - i_3 r_3 \Rightarrow i_3 = \left(\frac{\mathcal{E}_3}{r_3} - \frac{V}{r_3} \right) \quad \text{--- (3)}$$

$$V = \mathcal{E}_{eq} - i r_{eq} \Rightarrow i = \left(\frac{\mathcal{E}_{eq}}{r_{eq}} - \frac{V}{r_{eq}} \right) \quad \text{--- (4)}$$

$$i = i_1 + i_2 + i_3$$

$$\frac{\mathcal{E}_{eq}}{r_{eq}} - \frac{V}{r_{eq}} = \left(\frac{\mathcal{E}_1}{r_1} + \frac{\mathcal{E}_2}{r_2} + \frac{\mathcal{E}_3}{r_3} \right) - V \left(\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3} \right)$$


$$\frac{\mathcal{E}_{eq}}{R_{eq}} = \frac{\mathcal{E}_1}{R_1} + \frac{\mathcal{E}_2}{R_2} + \frac{\mathcal{E}_3}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

> The Junction Law:-

" Sum of current entering at junction = Sum of current leaving it "
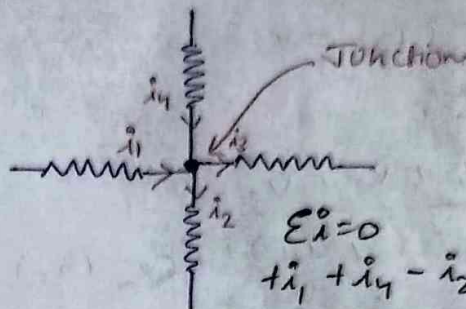
$$\therefore \hat{i}_4 + \hat{i}_4 = \hat{i}_2 + \hat{i}_3$$




$$\mathcal{E}i = 0$$

$$+i_1 + i_4 - i_2 - i_3 = 0$$


$$\therefore \hat{i}_1 + \hat{i}_4 = \hat{i}_2 + \hat{i}_3$$

> Sign Convention:-

(I)

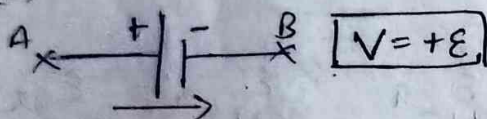


(V)

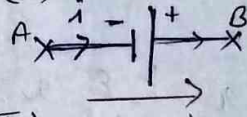


$$V = -E \quad \text{discharging phase!}$$

(II)

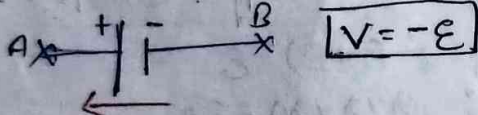


(VI)

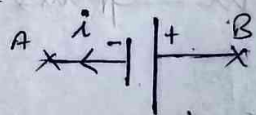


$$V = -E \quad \text{charging phase!}$$

(III)

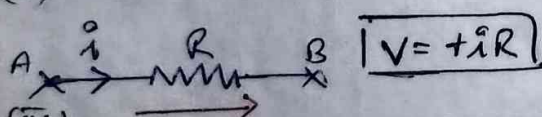


(VII)

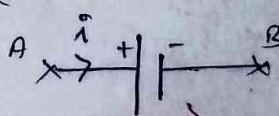


$$V = +E$$

(IV)

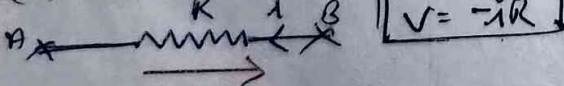


(VIII)

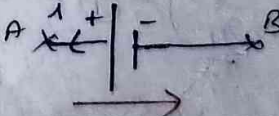


$$V = +E$$

direction of current does not matter in finding potential drop

(IX)

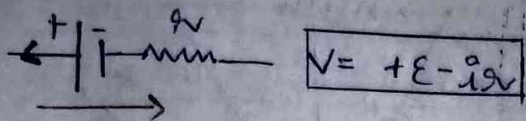


(X)

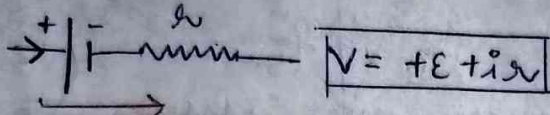

(XI)




(XII)

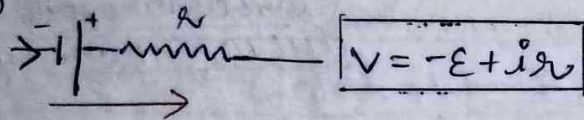


> The loop or voltage law :- (KVL)

The algebraic sum of all potential diff along closed loop in a circuit is zero
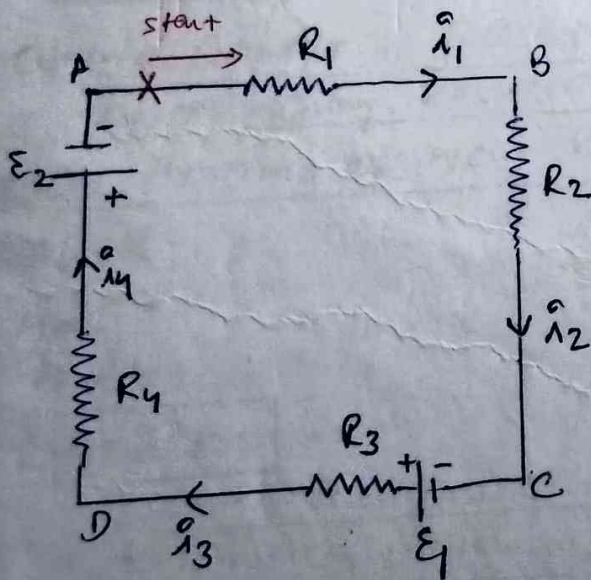
$$+i_1 R_1 + i_2 R_2 - E_1 + i_3 R_3 - i_4 R_4 + E_2 = 0$$




Methods of Symmetry :-

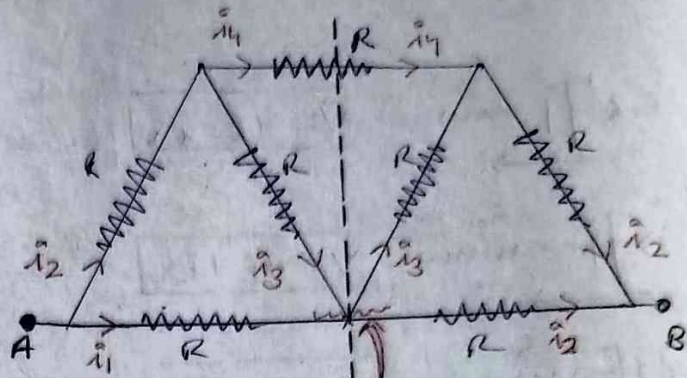

This connection can be removed due to symmetry

Delta to Star :-

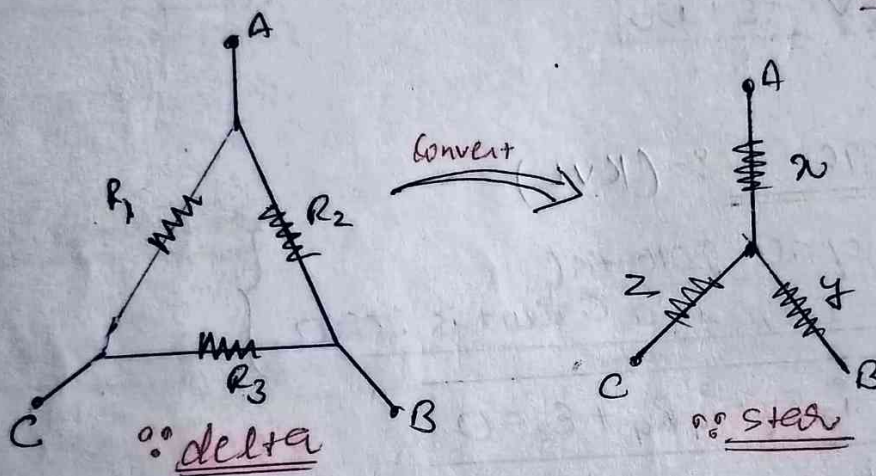

$$Z = \frac{R_1 R_2}{(R_1 + R_2 + R_3)}$$

$$Y = \frac{R_2 R_3}{(R_1 + R_2 + R_3)}$$

$$X = \frac{R_1 R_3}{(R_1 + R_2 + R_3)}$$

∴ Heating effect of Current :- (Electrical E → Heat E)

> The energy liberated / second :- Power
(work done in a battery / unit time)

$$P = \frac{dw}{dt} = \frac{dq(\Delta V)}{dt} = \left(\frac{dq}{dt}\right) \Delta V = iV$$

∴ $P = VI$

#


Electrical Pot. E lost in a device;

$$dU = (dQ)V = (i dt)(iR) = i^2 R dt$$

$$dU = i^2 R dt$$

$$\int dU = i^2 R \int dt$$

∴ $U = i^2 R t$

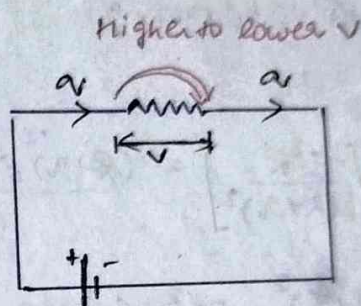

> Joule's Law of electrical heating :-


When a current is passed through a device having resistance R, then amount of heat produced;

$$H \propto R$$

$$H \propto i^2$$

$$H \propto t$$

∴ $H = i^2 R t$

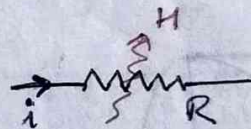

#

$$1 \text{ kWh} = 3.6 \times 10^6 \text{ J} = 10^7 \text{ J}$$

$$\frac{1 \text{ BTU}}{\text{British Thermal Unit}} = 1055 \text{ J}$$

#

Power

Series

$$\frac{P_1 P_2}{(P_1 + P_2)}$$


Parallel

$$(P_1 + P_2)$$

> Max. Power Transfer Theorem :-

Current delivered by Battery: $i = \frac{E}{R+r}$

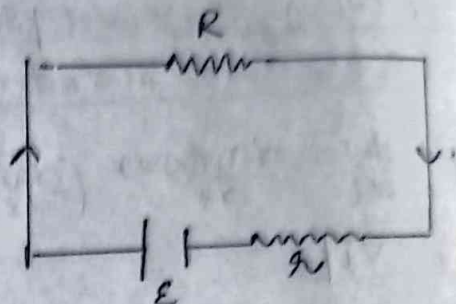Power dissipated across R : $i^2 R = \frac{E^2 R}{(R+r)^2}$



for P to be max:

$$\frac{dP}{dR} = 0$$


$$\frac{d}{dR} \left[\frac{E^2 R}{(R+r)^2} \right] = \frac{(R+r)^2 E^2 - E^2 R [2(R+r)]}{(R+r)^4} = 0$$

$$E^2 (R+r)^2 - 2E^2 R (R+r) = 0$$

$$E^2 (R+r) [R+r - 2R] = 0$$

$$R - r = 0 \Rightarrow \boxed{R = r}$$

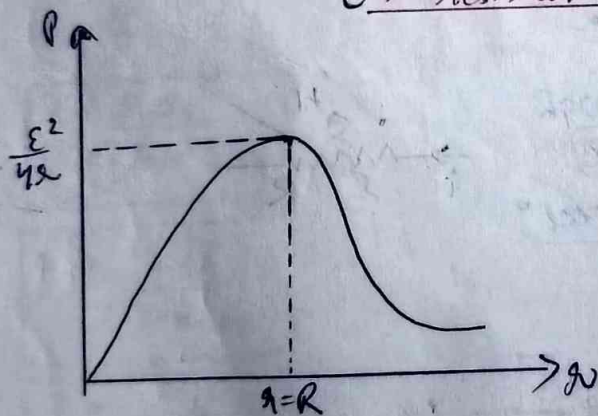(Ext. resistor = int. resistor of Battery)




> RC-charging Circuit :-

Equation of loop:

$$iR + \frac{q}{C} - E = 0$$

$$iR = \frac{CE - q}{C}$$

$$\frac{dq}{dt} = \frac{CE - q}{RC}$$

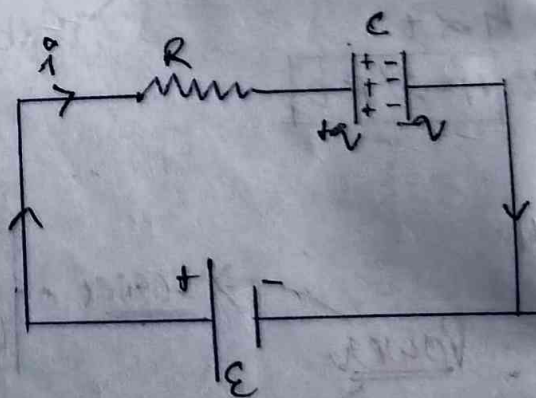

$$\frac{dV}{EC - V} = \frac{dt}{RC}$$

$$\int \frac{1}{(EC - V)} dV = \int \frac{1}{RC} dt$$

$$[-\ln(EC - V)]_0^V = \left[\frac{t}{RC}\right]_0^t$$

$$\ln(EC - V) - \ln(EC) = -\frac{t}{RC}$$

$$\ln\left(\frac{EC - V}{EC}\right) = -\frac{t}{RC}$$

$$\frac{EC - V}{EC} = e^{-t/RC}$$

$$1 - \frac{V}{EC} = e^{-t/RC}$$

$$\therefore \boxed{V = EC(1 - e^{-t/RC})} \checkmark$$

$$i = \frac{dV}{dt} = \frac{d}{dt} [EC(1 - e^{-t/RC})]$$

$$i = +\frac{EC}{RC} e^{-t/RC}$$


$$\therefore \boxed{i = \frac{E}{R} e^{-t/RC}} \checkmark \rightarrow \text{Time Constant}$$

$$T = RC$$

$$At^0, t = T$$

$$i = \frac{E}{R} \left(\frac{1}{e}\right) = 0.37 \frac{E}{R}$$

$$\boxed{i = 0.37 E/R}$$

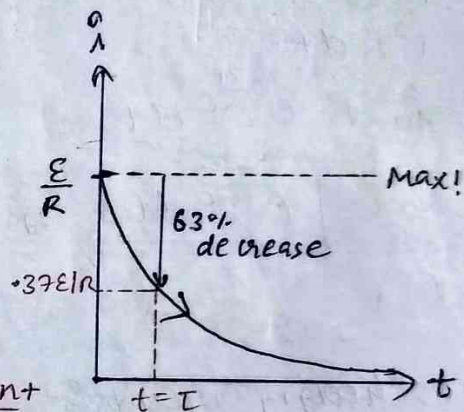

#

$$V_{\text{resistor}} = iR$$

$$\Rightarrow \frac{E}{R} e^{-t/RC} \times R = E e^{-t/RC}$$

$$\boxed{V_R = E e^{-t/RC}}$$

#

$$V_{\text{capacitance}} = \frac{Q}{C} = \frac{EC(1 - e^{-t/RC})}{C}$$

$$\Rightarrow E(1 - e^{-t/RC})$$

$$\boxed{V_C = E(1 - e^{-t/RC})}$$


$$\therefore \underline{\underline{V_C + V_R = E}}$$

#

Energy stored in Capacitor :-

$$U = \frac{q^2}{2C} = \frac{\epsilon^2 C^2 (1 - e^{-t/RC})^2}{2C} = \frac{1}{2} \epsilon^2 C (1 - e^{-t/RC})^2$$
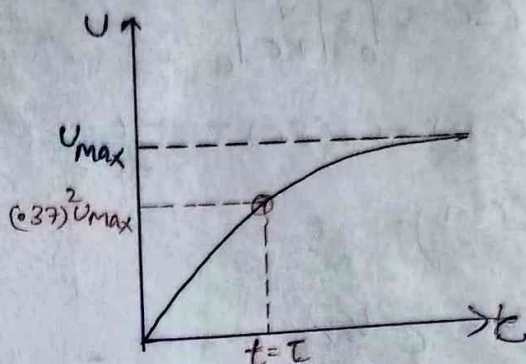
$$\therefore U_C = \frac{1}{2} C \epsilon^2 (1 - e^{-t/RC})^2$$



> Energy lost as heat :-

$$dH = i^2 R dt$$

$$dH = i_0^2 R e^{-\frac{2t}{RC}} dt$$

$$H = i_0^2 R \int e^{-\frac{2t}{RC}} dt = \left(\frac{\epsilon}{R}\right)^2 R \left[\frac{e^{-\frac{2t}{RC}}}{-\frac{2}{RC}} \right]_0^\infty = \frac{1}{2} C \epsilon^2$$

> R-C discharging circuit :-

$$+iR - \frac{q}{C} = 0$$

$$\Rightarrow iR = \frac{q}{C}$$

$$\Rightarrow \left(-\frac{dq}{dt} \right) = \frac{q}{RC}$$


Since the Cap.

is discharging

so, q (\downarrow) with time

then, $\frac{dq}{dt} < 0$
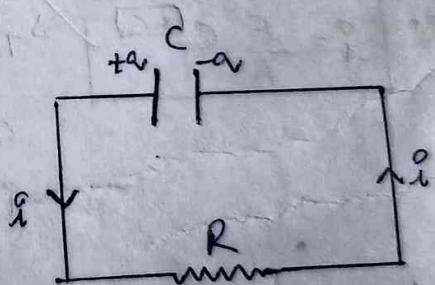
$$\Rightarrow \frac{dq}{q} = -\frac{dt}{RC}$$




$$\int_{a_0}^a \frac{da}{a} = - \int_0^t \frac{dt}{RC}$$

$$\ln\left(\frac{a}{a_0}\right) = \frac{-t}{RC}$$

$$\therefore a = a_0 e^{-t/RC}$$

$$\text{at } t = \tau$$

$$a = 0.37a_0 \quad \text{--- (1)}$$

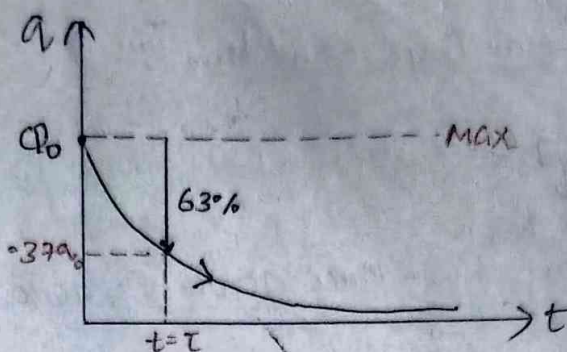


#

$$a = a_0 e^{-t/RC}$$

$$i = -\frac{da}{dt}$$

$$\Rightarrow -\frac{d}{dt}(a_0 e^{-t/RC})$$
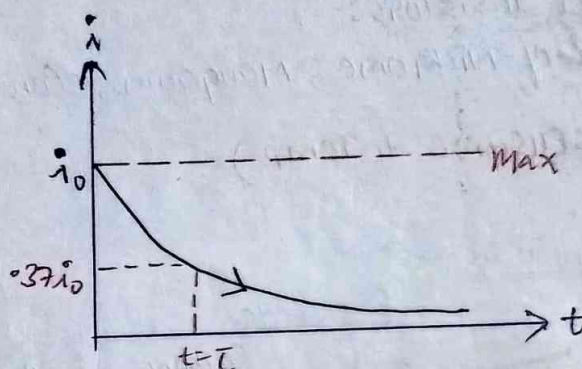
$$\therefore i = \frac{a_0}{RC} e^{-t/RC}$$



$$V_C = \frac{a}{C} = \frac{a_0}{C} e^{-t/RC}$$

$$V_R = iR = (i_0 R) e^{-t/RC} = \frac{a_0}{C} e^{-t/RC}$$

$$\therefore V_C = V_R \quad \therefore$$

Energy stored in Cap (U) = $\frac{a^2}{2C} = \frac{a_0^2}{2C} e^{-\frac{2t}{RC}}$; at $t=0$ $U = \frac{a_0^2}{2C}$

Energy lost as heat (dH) :-

$$dH = i^2 R dt$$

$$= i_0^2 R e^{-\frac{2t}{RC}} dt$$

$$H = i_0^2 R \int_0^\infty e^{-\frac{2t}{RC}} dt = \frac{i_0^2 R}{2/RC} (e^{-\infty} - (-e^0)) = \frac{a_0^2}{2C}$$

The stored energy is lost as heat completely.

$$\frac{a_0^2}{2C}$$

Equivalent Time Constant :-

$$T = R_{eq} C$$

where R_{eq} is

Equivalent Resistance across Capacitor!


> TYPE OF RESISTORS :-

(i) Wired resistors :-

(Made of Nichrome, Manganin, Constantan)

(less sensitive to Temp.)

(ii) Carbon resistors :-

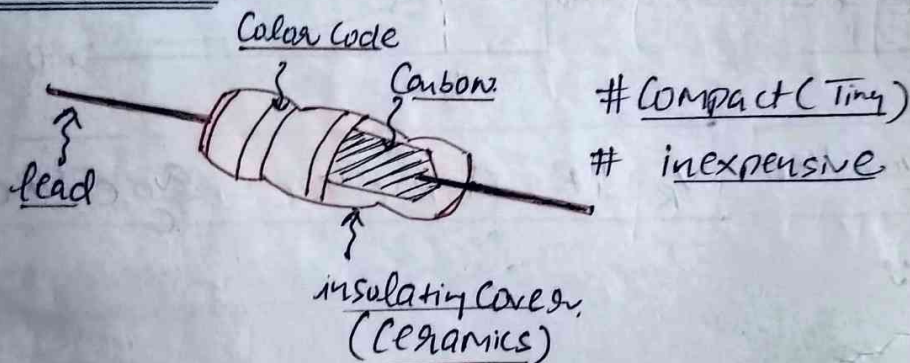

> Color Codes :-

	Number	Multiplier
Black ✓	0	10^0
Brown ✓	1	10^1
Red ✓	2	10^2
Orange ✓	3	10^3
Yellow	4	10^4
Green	5	10^5
Blue	6	10^6
Violet	7	10^7
Gray	8	10^8
White	9	10^9

B B ROY OF
GREAT BRITAIN
HAD A VERY
GOOD WIFE
WHO WORE GOLD
AND
SILVER NECKLACE

> Tolerance :-

	NO°	Multiplier	Tolerance
<u>Gold</u>	-	10^{-1}	5%
<u>Silver</u>	-	10^{-2}	10%
<u>NO Colour</u>	-	-	20%